



**Assignment 2** - Digital Electronics and Computer Organization Laboratory- ENCS2110

---


**Q1) Implement the following Boolean expression using Mux 4\*1 and other gates if needed. (2 points)**

a)  $F = A' + BC' + A'C$

**Q2) Implement the following Boolean expression using Decoder 3\*8. (2 points)**

a)  $F = A'C' + AC + BD + B'D$

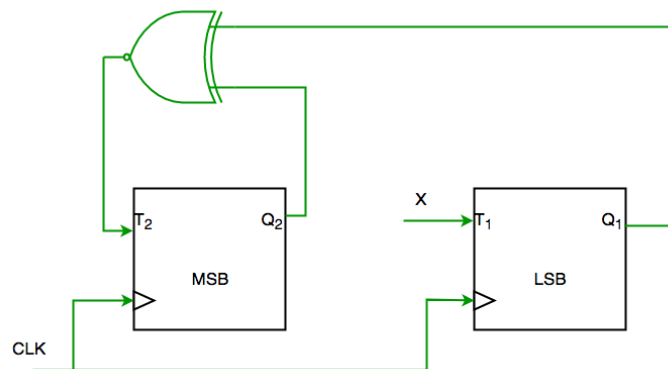**Q3) What is the output for the first five cycles of the following circuit if the input X is initially 1. (2 points)**



**Q4) Design a 3-bit synchronous counter circuit via using JK flip flop. (2 points)**

**Q5) Draw the four possible scenarios for the 3-bit shift register. For each scenario, determine the number of clock cycles required for both reading and writing. (2 points)**